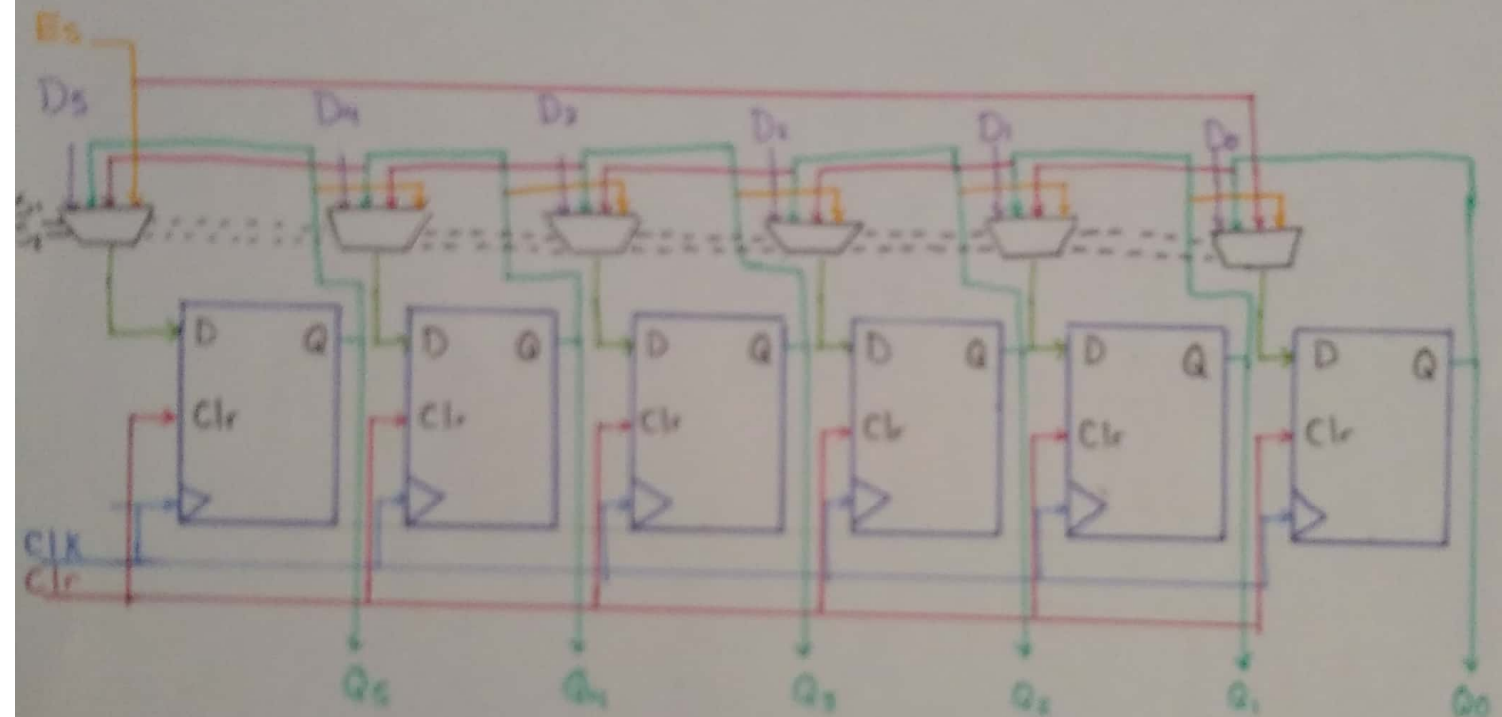


Córdova Pichardo Francisco Uriel

Registro generico de 6 bits



Practica 3

```
1 library ieee;
2 use ieee.std_logic_1164.all;
3
4 entity PRegistros is port
5 (
6     d : in std_logic_vector(6 downto 0);
7     es, clk, clr : in std_logic;
8     oper : in std_logic_vector(1 downto 0);
9     q : out std_logic_vector(6 downto 0)
10 );
11 end PRegistros;
12
13 architecture ARegistros of PRegistros is
14 begin
15     process(clk, clr)
16     begin
17         if(clr = '1') then
18             q <= "00000000";
19         elsif (rising_edge(clk)) then
20             if(oper="00") then --retencion
21                 q<=q;
22             elsif(oper = "01") then --carga
23                 q <= d;
24             elsif(oper = "10") then --corrimiento ala izquierda
25                 for i in 0 to 6 loop
26                     if(i > 0) then
27                         q(i)<=q(i-1);
28                     end if;
29                 end loop;
30             elsif(oper = "11") then --corrimiento a la derecha
31                 for i in 0 to 6 loop
32                     if(i < 5) then
33                         q(i) <= q(i+1);
34                     else
35                         q(i) <= es;
36                     end if;
37                 end loop;
38             end if;
39         end if;
40     end process;
41 end ARegistros;
```

C22V10


```

clk =| 1|
es =| 2|
d(6) =| 3|
d(5) =| 4|
d(4) =| 5|
d(3) =| 6|
oper(1) =| 7|
oper(0) =| 8|
d(2) =| 9|
d(1) =|10|
d(0) =|11|
not used *|12|
|24| * not used
|23| = q(5)
|22| = q(3)
|21| = q(1)
|20| * not used
|19| * not used
|18| * not used
|17| = q(0)
|16| = q(2)
|15| = q(4)
|14| = q(6)
|13| = clr

```

Entrada d= 1001111


Corrimiento a la derecha

 

Salida q=1100111, 1100111, 1110011, 1111001, 1111100, 1111110, 1111111


Corrimiento a la izquierda

Entrada d=1001111

 


Salida q=1001111, 0011111, 0111111, 111111

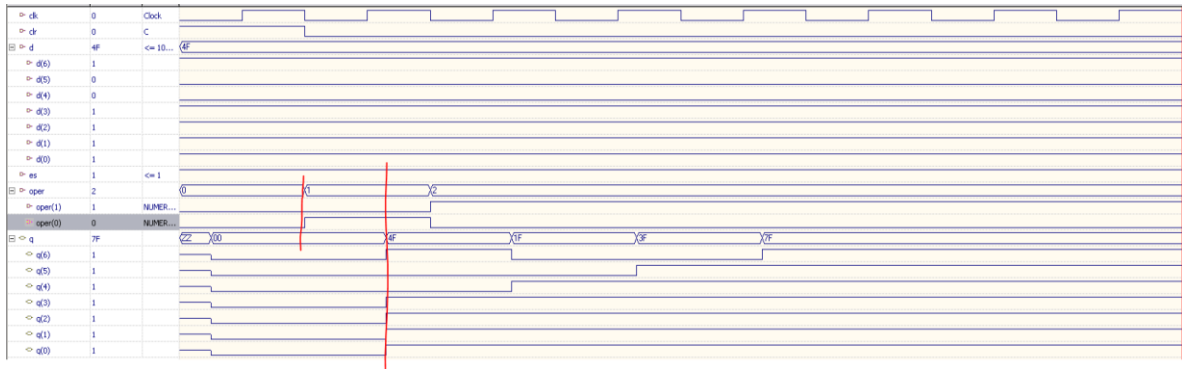
La carga de bits se ve en este punto en ambas simulaciones en el flanco de ascenso




Retención de bits

 


Simulación proteus

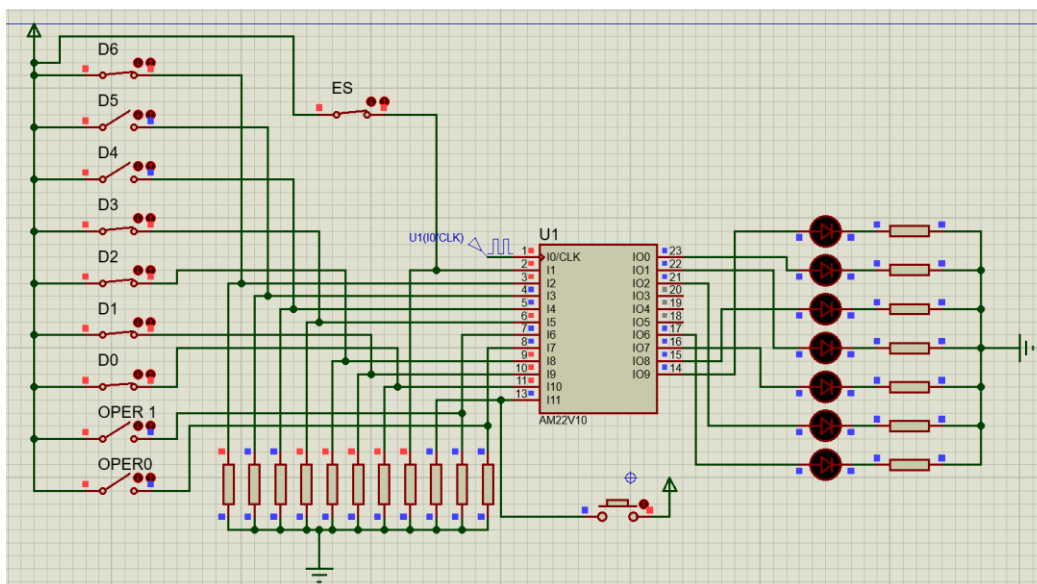



Carga de bits


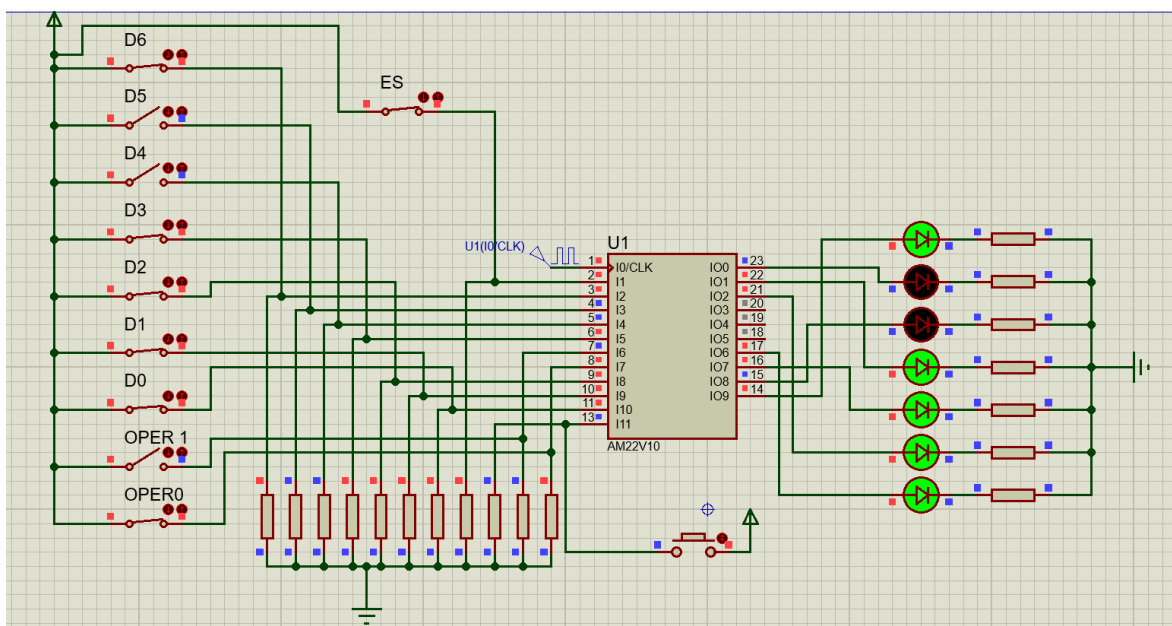




Retención de bits

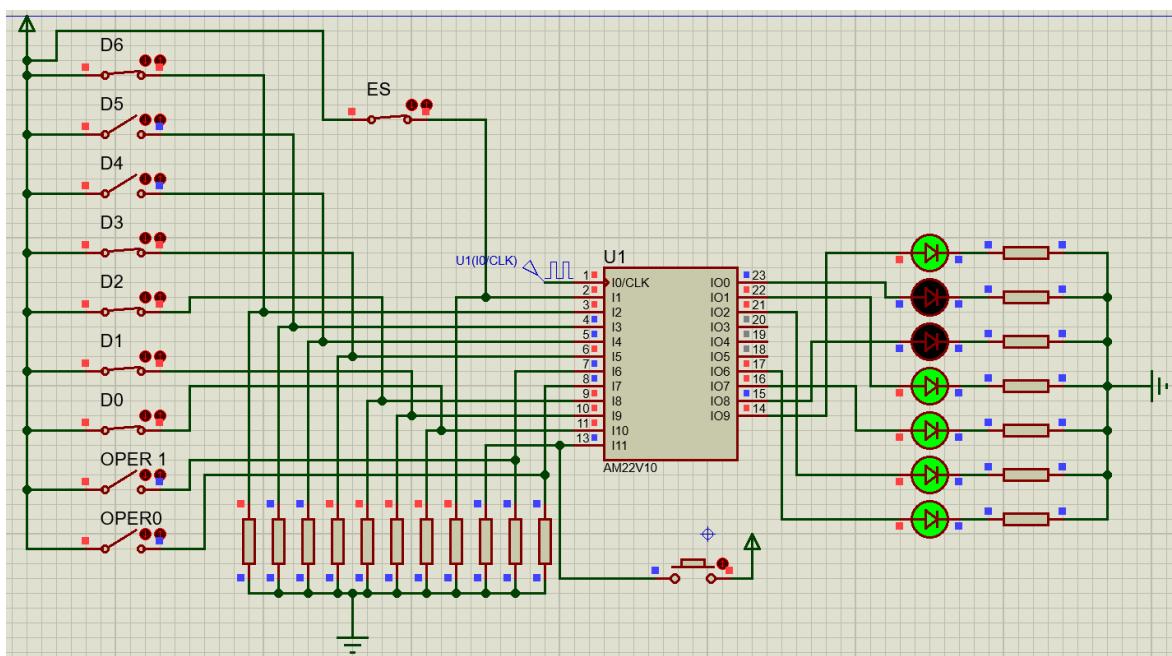

Corrimiento a la derecha

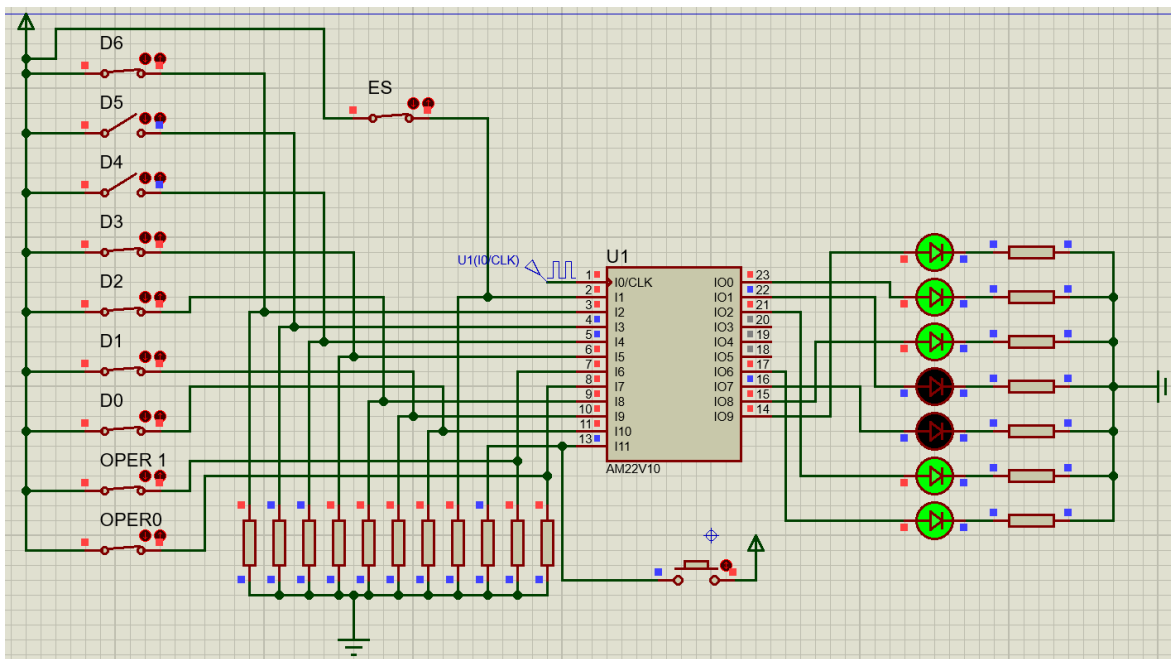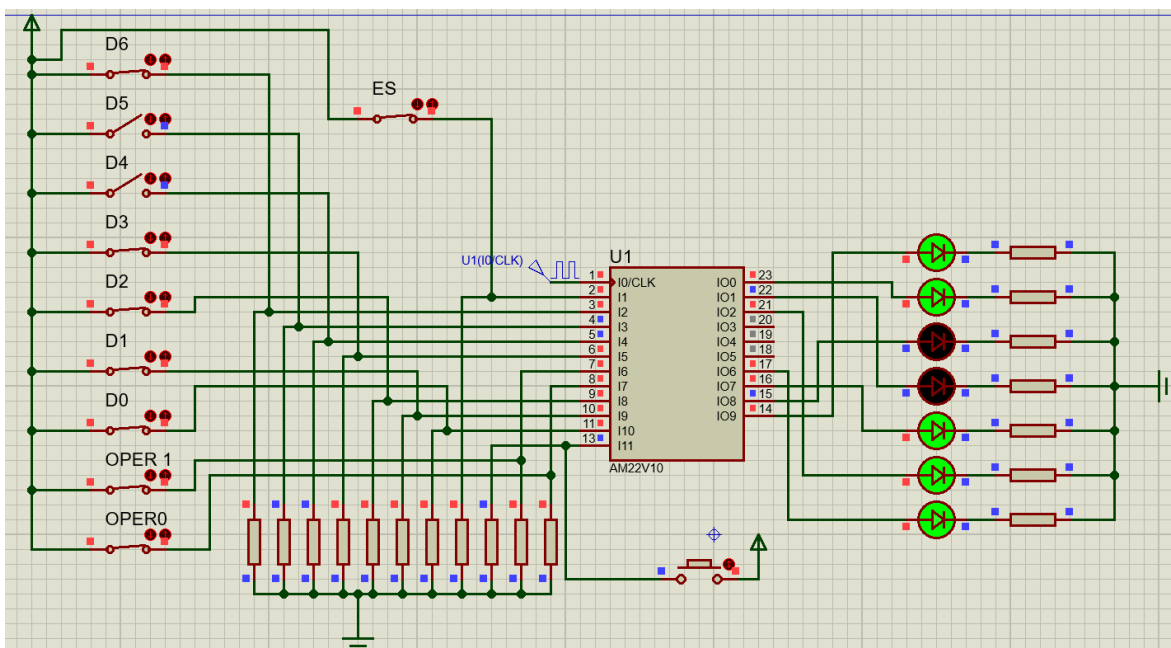

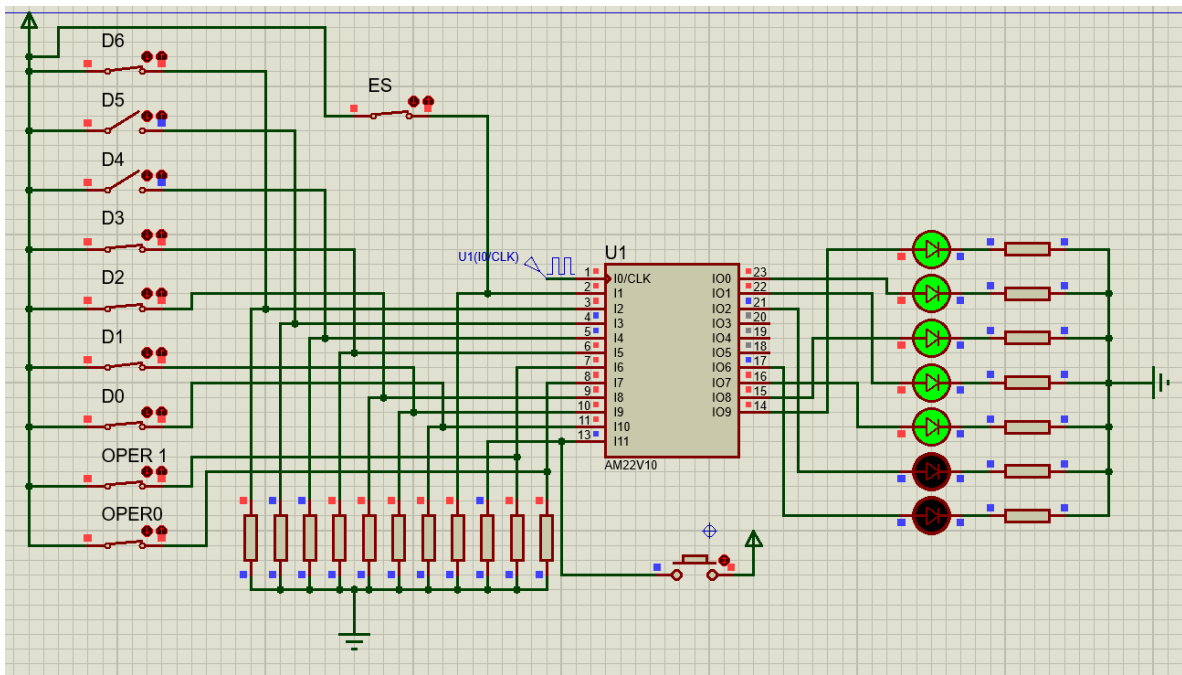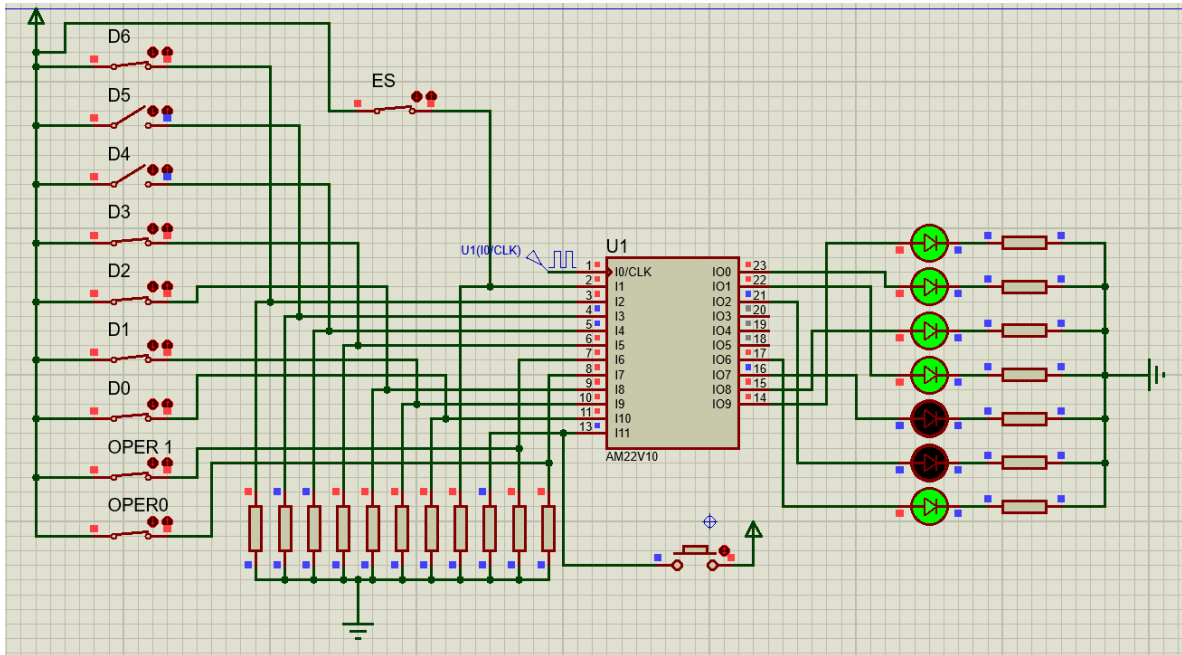

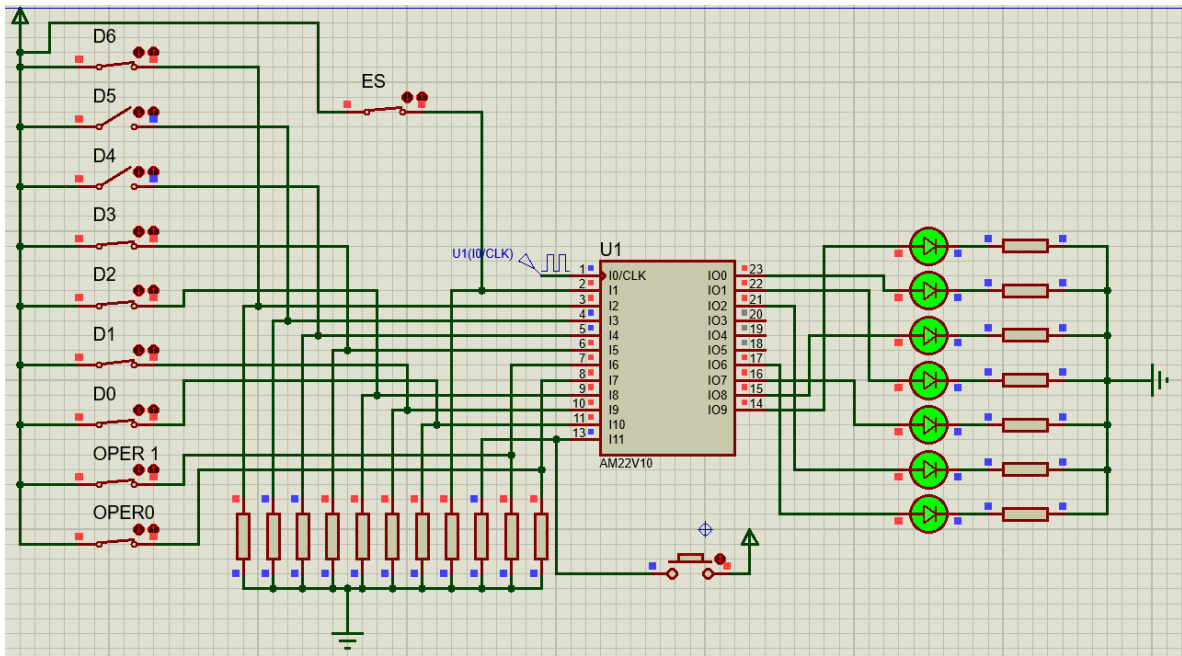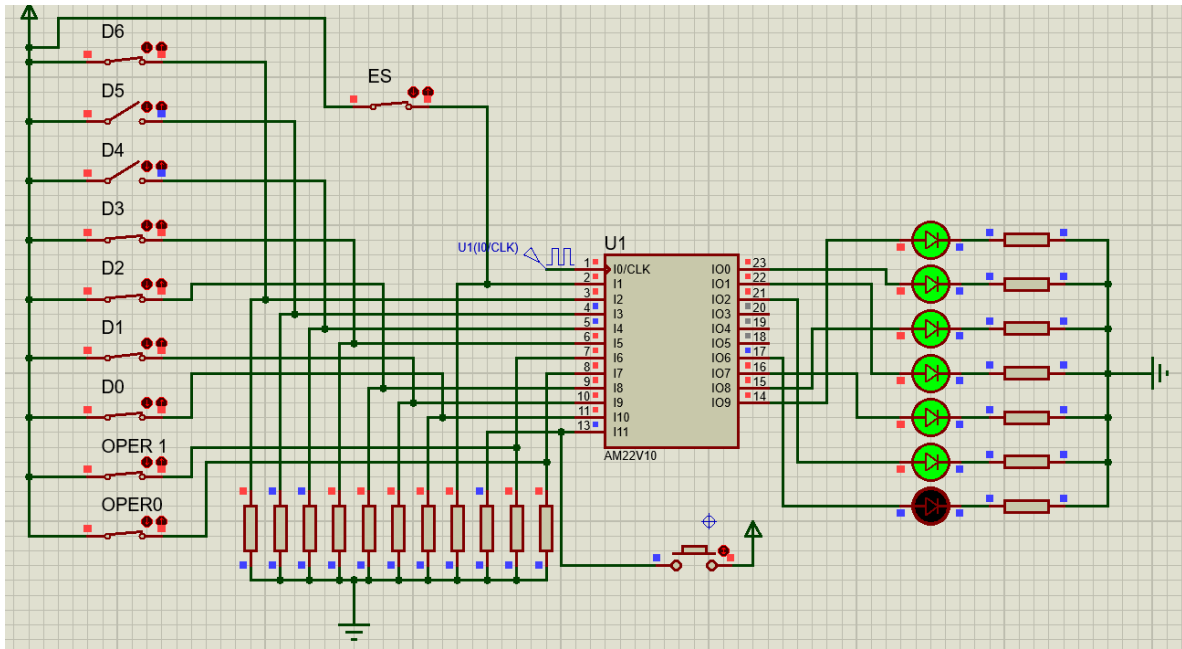

Corrimiento a la izquierda

